



Department of
Electrical & Electronic Engineering
Independent University, Bangladesh

Faiyaz Ahmed
1820545

Objective: Design an Analog MOS Amplifier (common-source, single stage) with voltage gain 30dB using a 180nm process with different biasing techniques. Compare performance for each of the design in terms of power consumption, area, frequency response (gain vs frequency) and noise robustness.

Note: The major goal of “Bias” is to ensure that MOS is in saturation at all times. Bias point should be stable (i.e., resilient to variations in $\mu_n C_{ox}$ (W/L), V_t , ... due to temperature and/or manufacturing variability.) Important parameters are I_D and V_{DS} . Bias point impacts the small-signal parameters. Bias point impacts how large a signal can be amplified. Bias point impact power consumption.

The noise sources in MOSFETs include:

(a) thermal noise

introduced by the channel;

(b) flicker noise from the channel;


(c) thermal noise introduced by the polysilicon gate resistance;

(d) thermal noise introduced by the source/drain resistance and

(e) thermal noise introduced by the distributed substrate resistance.

1) *Biasing by fixing V_{GS}*


Bias with Gate Voltage

 


$$I_D = 0.5\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

$$V_{DS} = V_{DD} - I_D R_D$$


$$W/L=10$$

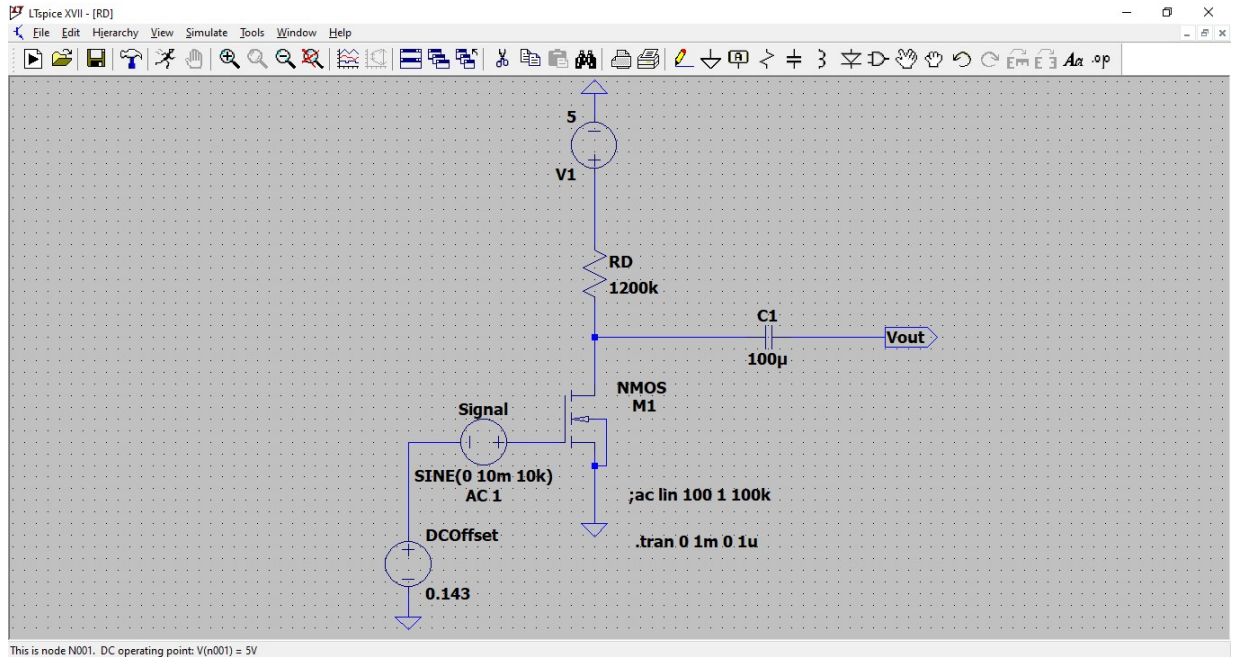

 a) Frequency response (gain vs frequency)



b) Power consumption

 

Power consumption = 5.1581 μW

- c) Area = $1.5 \cdot W \cdot L = 0.486 \text{ um square}$ + resistor area + source area
- d) Noise Robustness: Susceptible to dc noise



❖ Discussion:

- This method is NOT desirable as $\mu nCox$ (W/L) and V_t are not “well-defined.” Bias point (i.e., I_D and V_{DS}) can change drastically due to temperature and/or manufacturing variability.


2) Biasing using a Drain-to-Gate Feedback Resistor

$W/L=10$


Drain Feedback

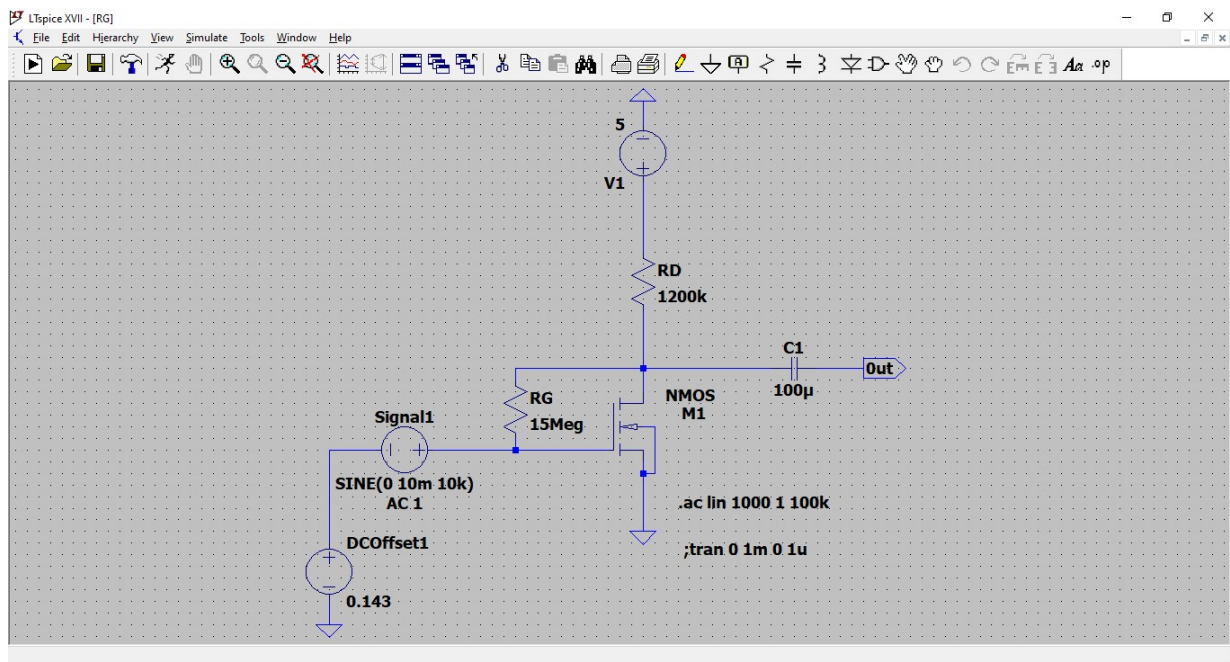 

 a) Frequency response (gain vs frequency)



b) Power Consumption

 

Power Consumption=4.7979 μ W

c) Area = $1.5 * W * L = 0.486 \text{ um square}$ + resistor area + sources area

d) Noise Robustness: Susceptible to DC noise

❖ **Discussion:**

- Here the large feedback resistance R_G in, Meg range, forces DC voltage at the Gate to be equal to that at the drain because $I_G=0$, approximately.

Thus we can write

$$V_{GS} = V_{DS} = V_{DD} - R_D I_D$$


Which can be rewritten in the form

$$V_{DD} = V_{GS} + R_D I_D$$


- If I_D increases due to any reason, then V_{GS} must decrease
- The decrease in V_{GS} in turn causes a decrease in I_D
- Thus, the negative feedback by R_G keeps I_D reasonably constant

3) Biasing by fixing V_G and connecting a resistance in the Source [Degeneration Resistance]


$$W/L=10$$

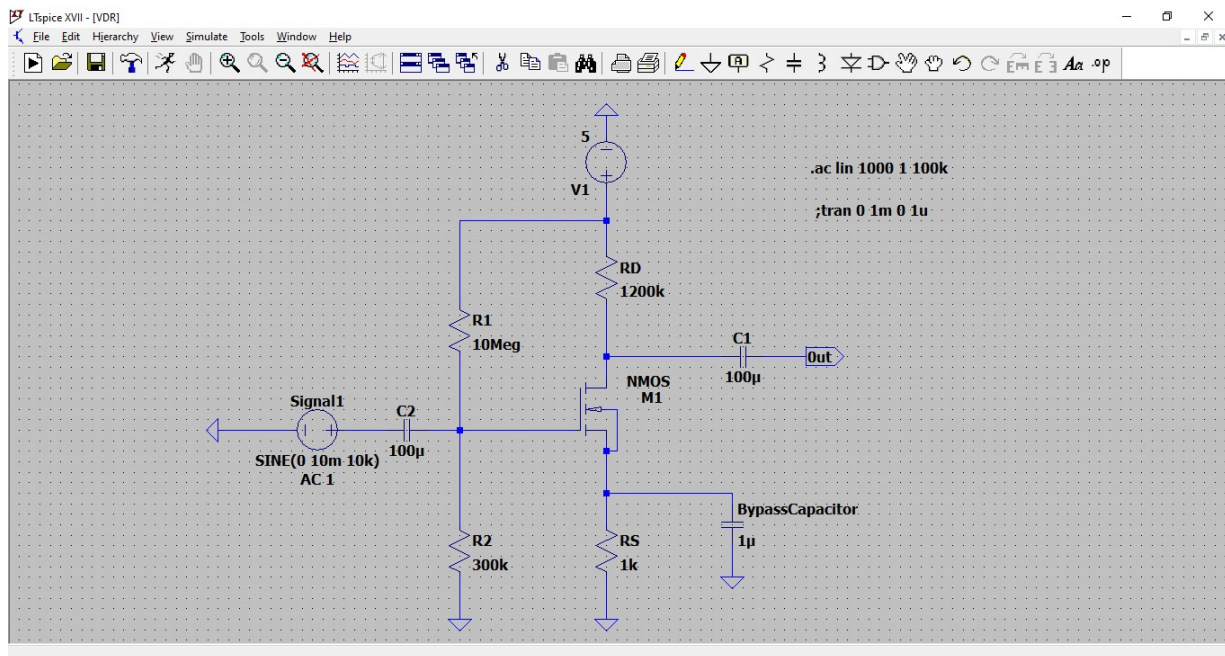

 a) Frequency response (gain vs frequency)



b) Power Consumption

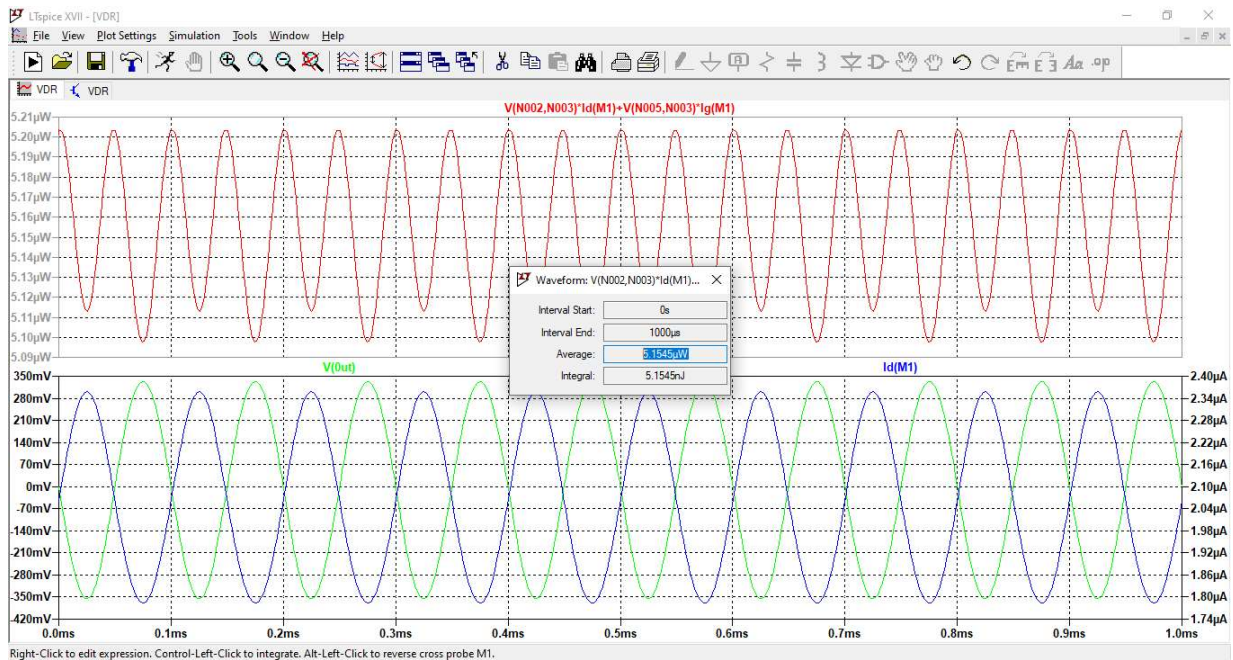

Power Consumption = 5.1545μW

c) Area = $1.5 \times W \times L = 0.486 \text{ um square}$

d) Noise: Due to capacitor coupling, not susceptible to DC noise

❖ Discussion

- Since $I_g=0$, R_1 and R_2 are selected to be very large in order to provide higher input gate resistance, and negligible current in the VDR branch such that power dissipation is negligible. Input and output coupling capacitors must be used in order to filter out DC voltage.
- Resistor R_s provides negative feedback which stabilizes the bias current I_D .
- I_D increases and V_G remains constant, hence, V_{GS} will decrease which will further decrease I_D .
- R_s works to keep I_D as constant as possible.


4) Biasing Using a Constant-Current Source

- It is often needed to find the value of R in order to achieve a desired I_{REF}
- To ensure I_D and V_{DS} would not change (e.g., due to temperature variation). One can force I_D to be constant using a current source.


- Designing I_{REF}

$$I_{REF} = \frac{V_{DD} - V_{GS} + V_{SS}}{R}$$

 
$$I_{REF} = \frac{1}{2} k'_n \frac{W_1}{L_1} (V_{GS} - V_t)^2$$



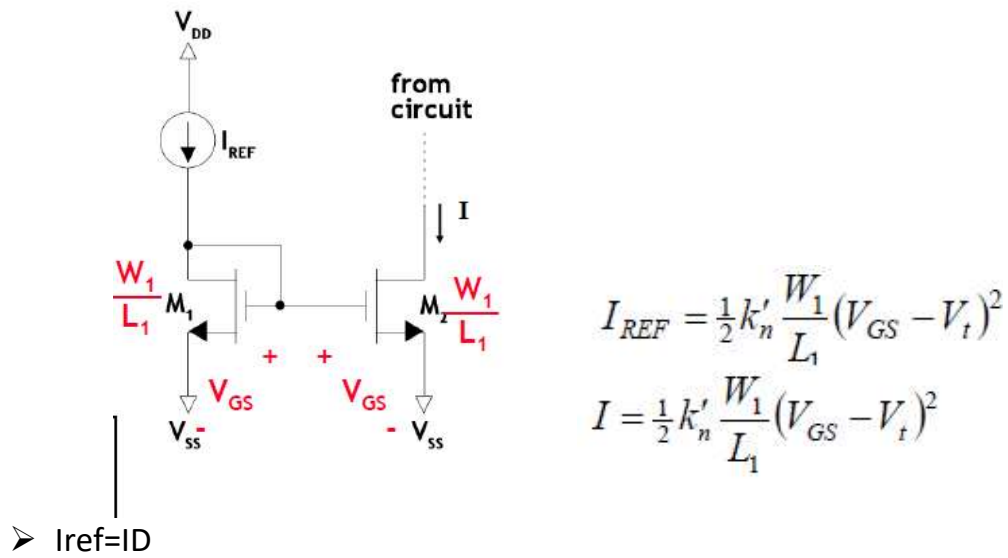- The width and length (the W/L aspect ratio) and the parameters of the two transistors *can be different*. We can choose W/L freely. In this circuit, consider W/L of both MOSFETs are the same and transistors are identical. The Gate-Source voltages are also the same, then



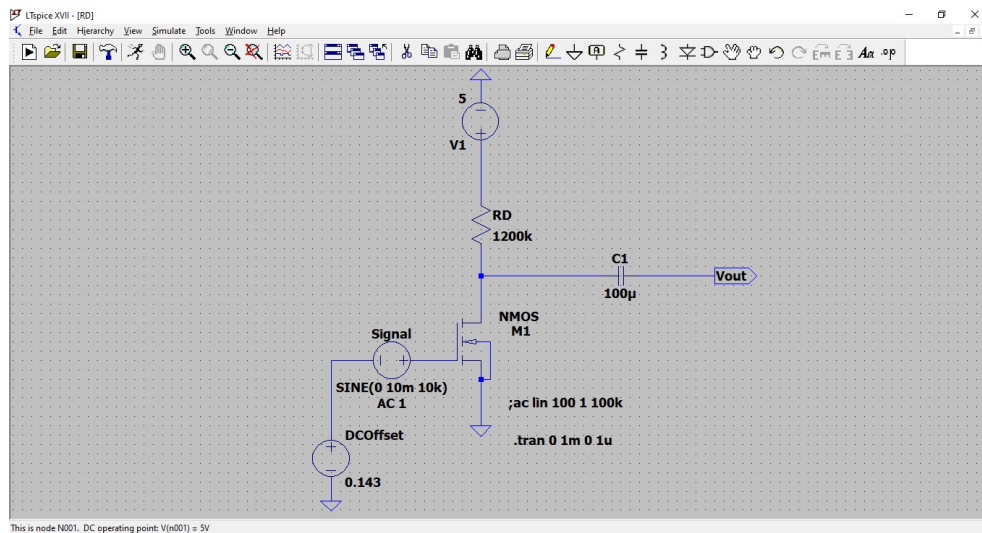Using the circuit [Biasing by Fixing V_{GS}] below to calculate I_D for Q-point,




DC Operating Point analysis,

```
* F:\Classroom\EEE 466 VLSI\Final\Faiyaz\RD.asc
--- Operating Point ---
V(n001):      5          voltage
V(n002):      2.54611    voltage
V(n004):      0.143      voltage
V(n003):      0.143      voltage
V(vout):      0.000254586 voltage
Id(M1):       2.04491e-006 device_current
Ig(M1):       0          device_current
Ib(M1):       -2.55611e-012 device_current
Is(M1):       -2.0449e-006 device_current
I(C1):        -2.54586e-016 device_current
I(Rd):        2.04491e-006 device_current
I(Signal):    0          device_current
I(Dcoffset):  0          device_current
I(V1):        -2.04491e-006 device_current
```


$I_D = 2.04491 \mu A$

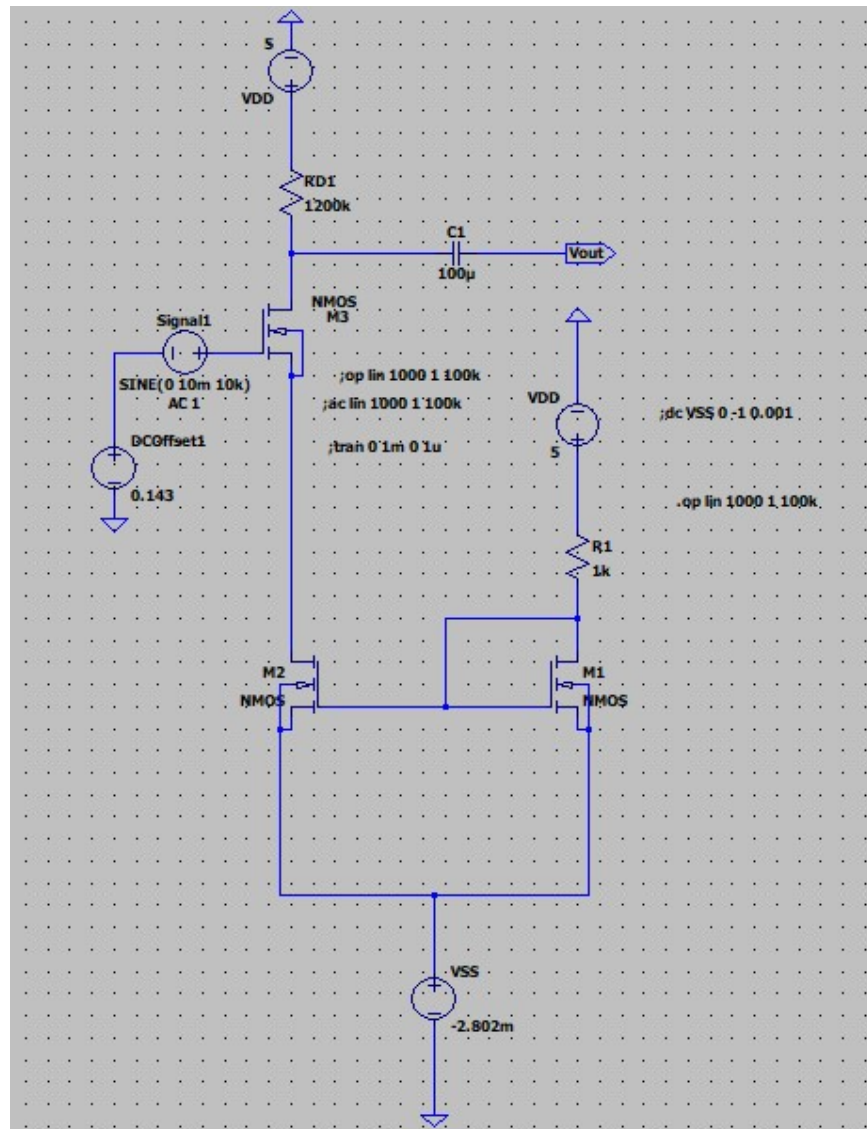Final circuit [after DC sweeping V_{ss} to find out the right value for which the current source supplies I_D at Q-point]:





W/L=10 [Same for all Mosfet]

 a) Frequency response (gain vs frequency)



b) Power Dissipation

 

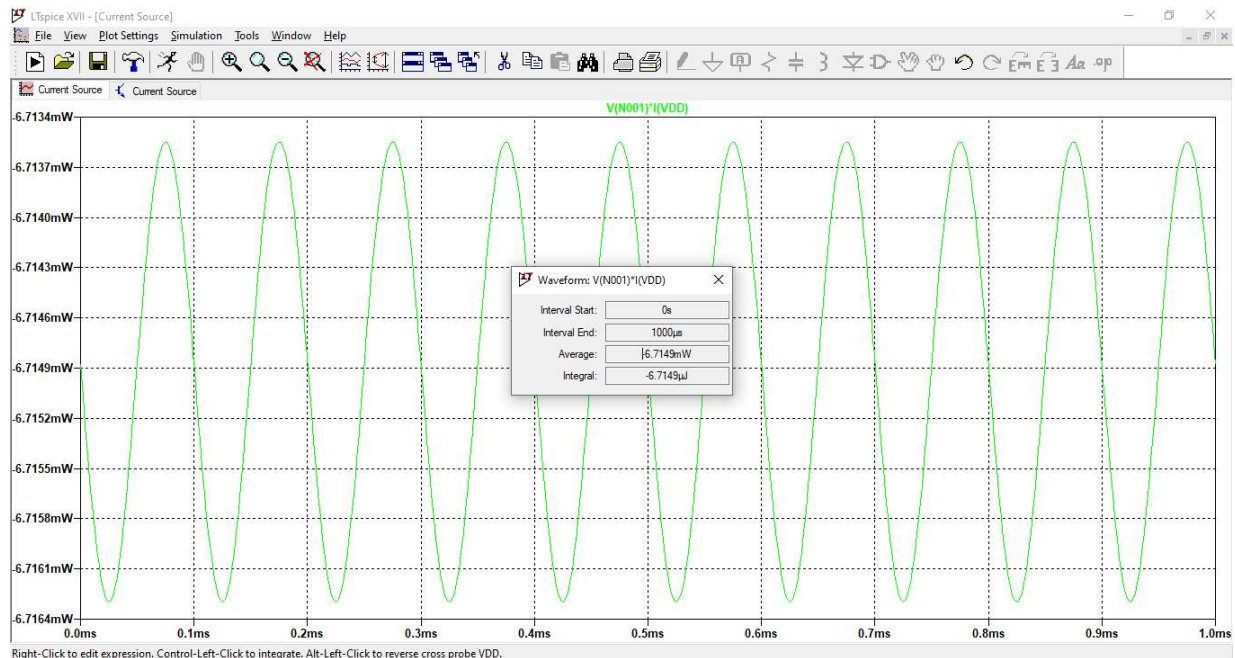

Power Dissipation = 6.7149mW

c) Area = $3 \times 1.5 \times W \times L = 1.458 \text{ um square} + \text{area of resistors}$

d) Noise Robustness: Highly susceptible to input DC noise without coupling capacitors

❖ Discussion

- The most effective biasing technique is using a constant current source.
- Resistor R_D establishes an appropriate voltage at drain to allow for the required output signal full swing while ensuring that the mosfet remains in the saturation region